



Boğaziçi University

**Introductory  
Phys Labs**

1863

# AMMETERS & VOLTMETERS

**PHYS 201**

A large, faint, circular seal of Boğaziçi University is centered in the background. The seal contains the text "BOĞAZIÇI ÜNİVERSİTESİ" around the top and "1863" at the bottom. In the center of the seal is a diamond-shaped emblem with a sun-like symbol inside.

# **THEORY AND APPARATUS**

# AMMETERS & VOLTMETERS

## AMMETER

An ammeter measures the electric current in a circuit. The name is derived from the Ampere (A), the base unit of electric current in SI.

In general, we do not want to disturb the system when we take measurements. To this end, we connect an ammeter in SERIES. Ideally, an ammeter has ZERO internal resistance, so when connected in series, it will not affect the circuit in any measurable way.

Although the ideal ammeter neither draws power nor reroutes currents, real ammeters necessarily do due to their nonzero internal resistance. Still, typically, the internal resistance is comparatively very low, so we neglect it for all practical purposes.



## AMMETERS & VOLTMETERS

### GALVANOMETER

The galvanometer is a device that detects an electric current. The value it reads is directly proportional to the current it measures.

The galvanometer has following applications:

- It is used for detecting the direction of electric current. It also determines the null (zero) point of the circuit, which is when no current flows.
- It is used for measuring a very small current.
- The voltage between any two points on the circuit may also be determined by a galvanometer.





## VOLTMETER

A voltmeter measures electric potential difference between two points in an electric circuit.

The ideal voltmeter has INFINITE internal resistance, and is connected in PARALLEL to the circuit element across which it measures a potential drop. This way, the voltmeter will not alter the original circuit.

An infinite internal resistance is not realizable, though. However, typically, voltmeters have comparatively very high internal resistances, so we treat them as infinite for all practical purposes.





# EXPERIMENT



# Part 1

## Procedure, Data, and Calculations

The following data are for demonstration purposes only.

**Part 1 will be done by Lab Instructor and the values obtained will be given to you!**




## DETERMINATION OF THE CONSTANTS OF A GALVANOMETER

The galvanometer internal resistance  $R_G$ , and the galvanometer current  $I_G$  are the galvanometer's constants.

Resistance is set to  $9999\Omega$  and decreased till you observe FSD on the galvanometer scale.  $R_1$  is read from Resistance Box 1.

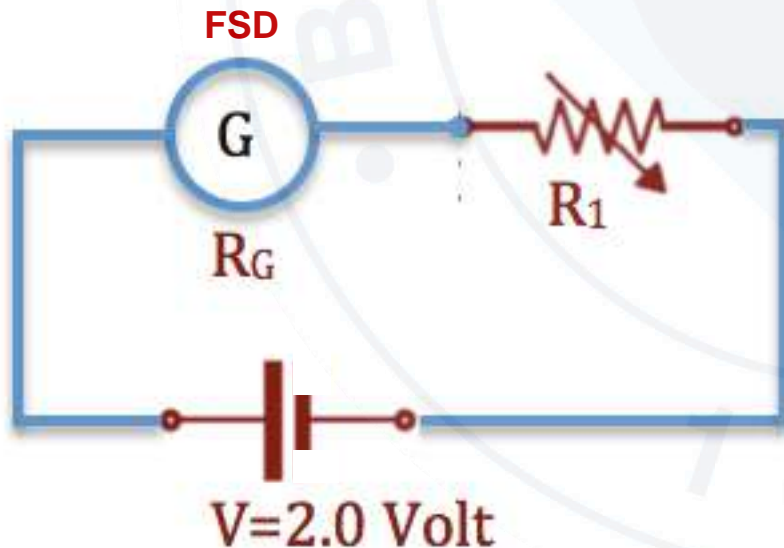This part will be done by Lab Instructor and the values obtained will be given to you!



# AMMETERS

This part will be done by Lab Instructor and the values obtained will be given to you!

Read  $R_1$  from the Resistor Box when FSD is observed.






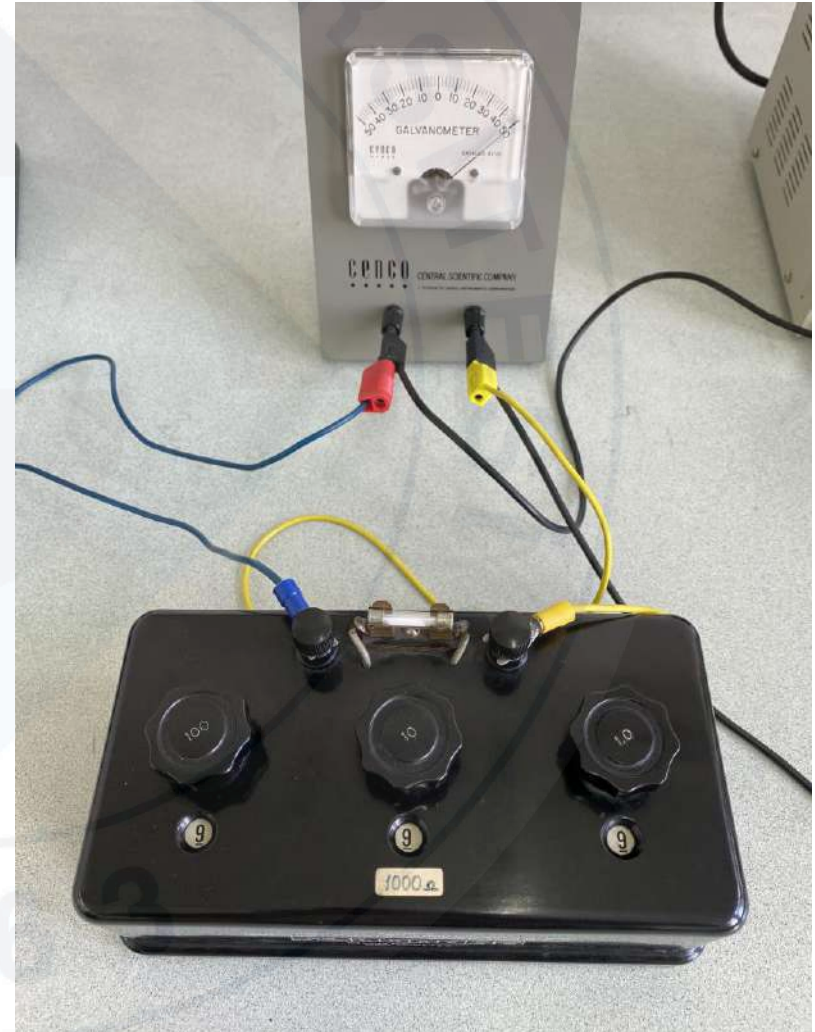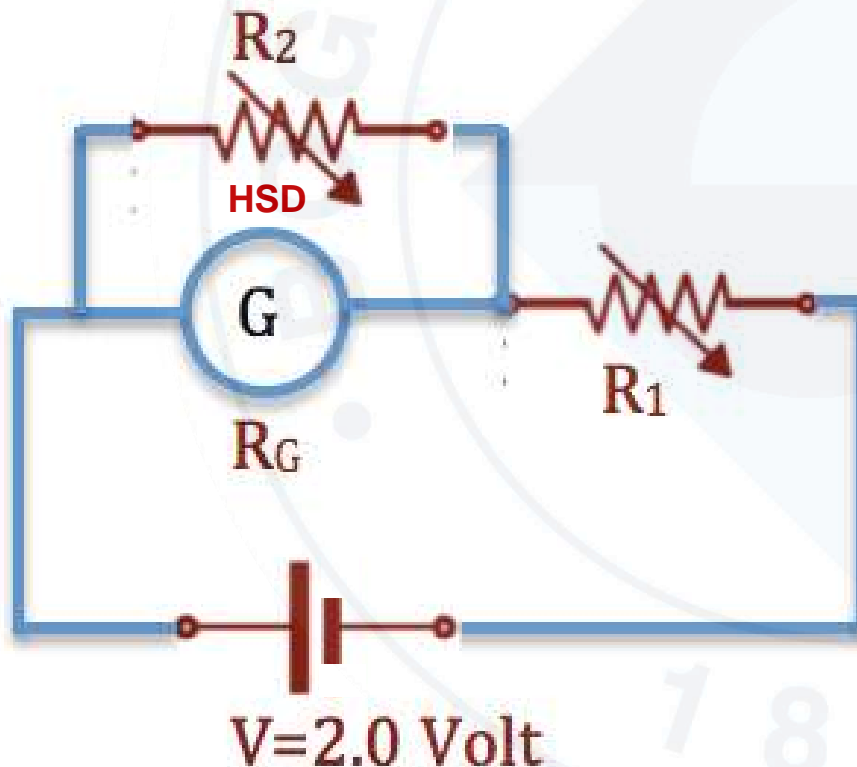
# AMMETERS

Set the parallel resistance to  $999\Omega$  and decrease it till you observe Half Scale Deflection (HSD) on the galvanometer scale.

This part will be done by Lab Instructor and the values obtained will be given to you!



# AMMETERS


$R_1$  and  $R_2$  are known

$(R_1 \gg R_2)$ .

Using the given circuit,  
determine  $R_G$ .

$R_G = ?$

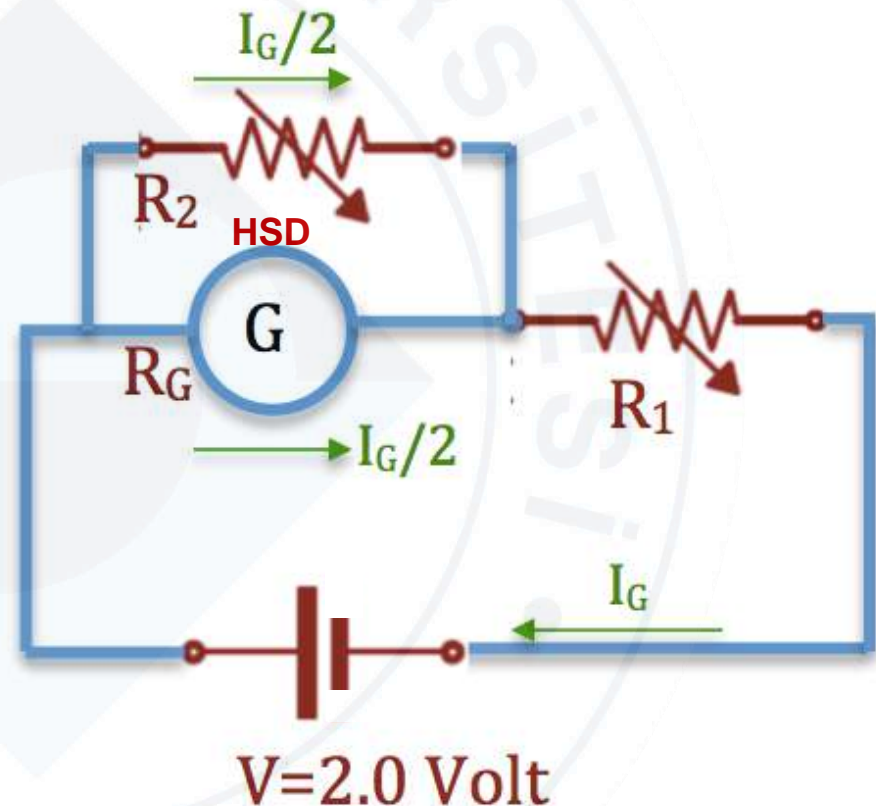
This part will be done by Lab  
Instructor and the values obtained  
will be given to you!


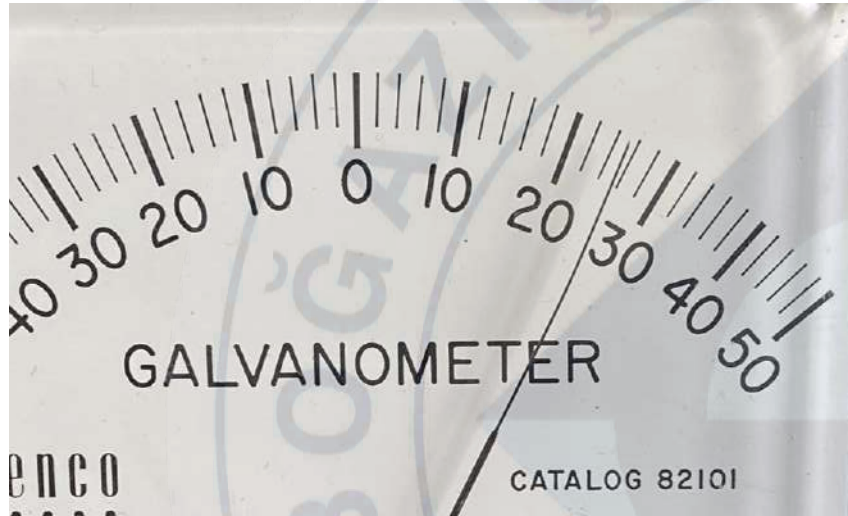
# AMMETERS

This part will be done by Lab Instructor and the values obtained will be given to you!

Observe Half Scale Deflection on the galvanometer scale. Read  $R_2$ .







# AMMETERS

$R_1$  and  $R_G$  are known. Using the given circuit determine  $I_G$ .

$I_G = ?$

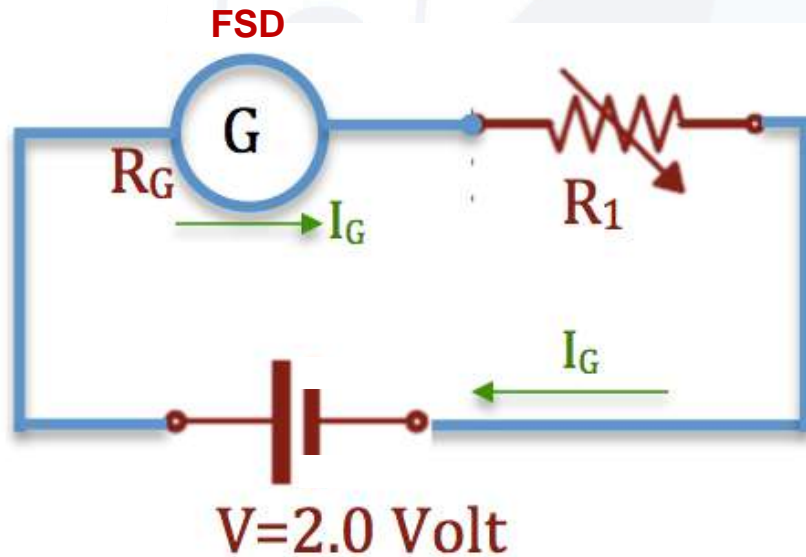

Description / Symbol	Formula / Value & Unit
Resistance to set for <b>FSD</b> $R_1 =$ .....	<b>You must calculate <math>I_G</math> yourself, it will not be given to you!</b>
Applied Potential $V_{app} =$ .....	
Resistance to set for <b>HSD</b> $R_2 =$ .....	<b>The other values will be given by your instructor!</b>
Internal resistance of the Galvanometer $R_G =$ .....	
Max. Galvanometer Current $I_G =$ .....	

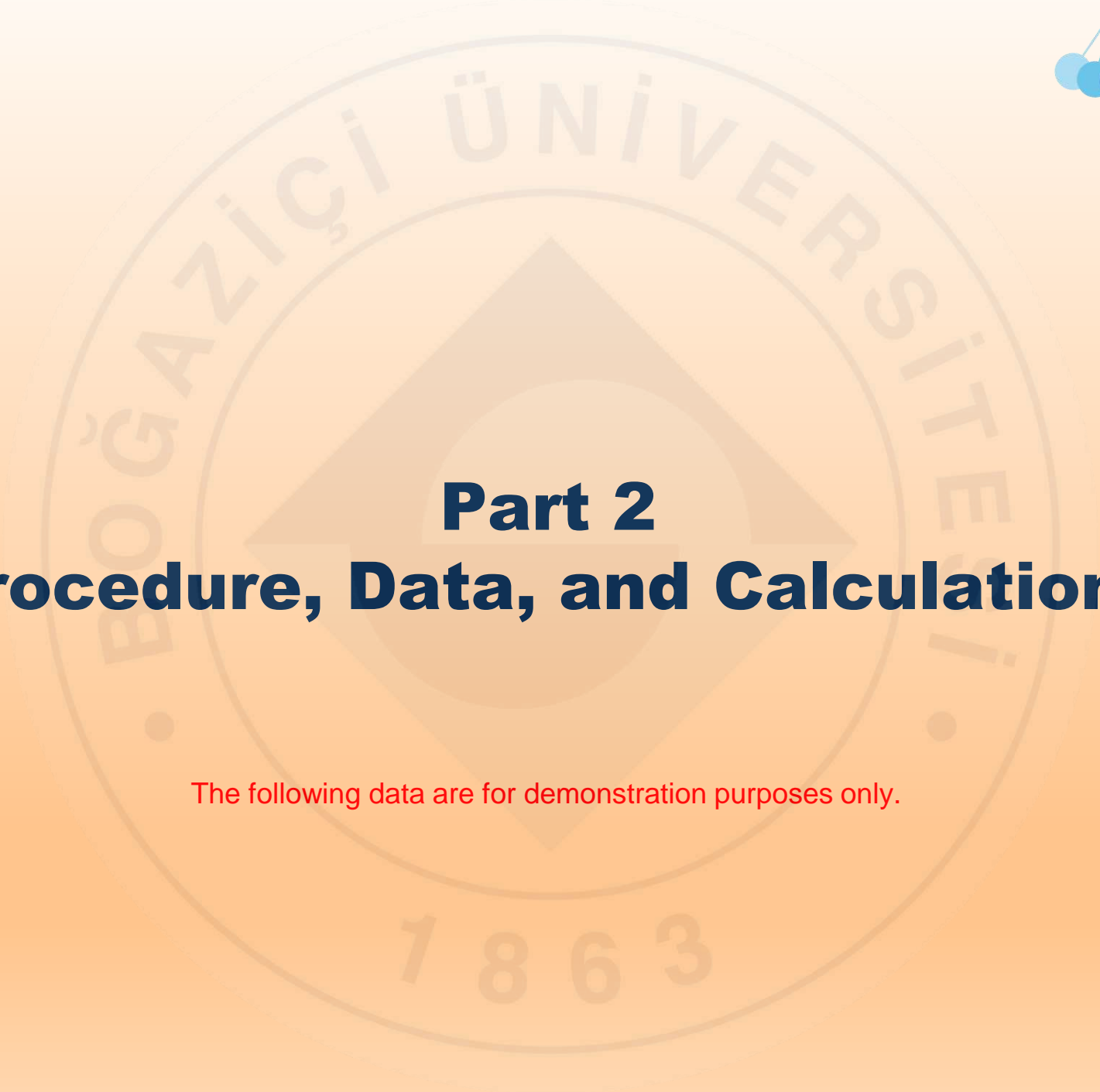The background features a large, faint watermark of the Boğaziçi University logo, which is a circular emblem containing a triangle and the text 'BOĞAZIÇI ÜNİVERSİTESİ' and '1863'.

# Part 2

## Procedure, Data, and Calculations

The following data are for demonstration purposes only.

## AMMETERS & VOLTMETERS

In order to build an ammeter, a sensitive galvanometer with an internal resistance of 50-100  $\Omega$  is used.

Before we construct our measuring device, we need to know the exact internal resistance of the galvanometer, and what current causes Full Scale Deflection (FSD).



Full Scale Deflection occurs when the pointer shows the maximum value on the scale. Here, the maximum value is 50, and the galvanometer is Full Scale Deflected.

The current causing FSD is called the Galvanometer Current,  $I_G$ .

## CONSTRUCTION OF AN AMMETER

In Part-1 we determined that the internal resistance of the galvanometer is neither zero nor infinite. So, we cannot use it directly as an ammeter. We must modify the galvanometer to suit our needs.

We will construct an ammeter that measures a maximum of  $I_R$  (will be given). That means the galvanometer we use to build an ammeter will Full Scale Deflect when it reads  $I_R$ .


We should remember that the galvanometer current,  $I_G$ , causes Full Scale Deflection and is much smaller than the range current,  $I_R$ .

## CONSTRUCTION OF AN AMMETER

We will construct an ammeter which measures maximum a given  $I_R$ .

$$I_R \gg I_G$$

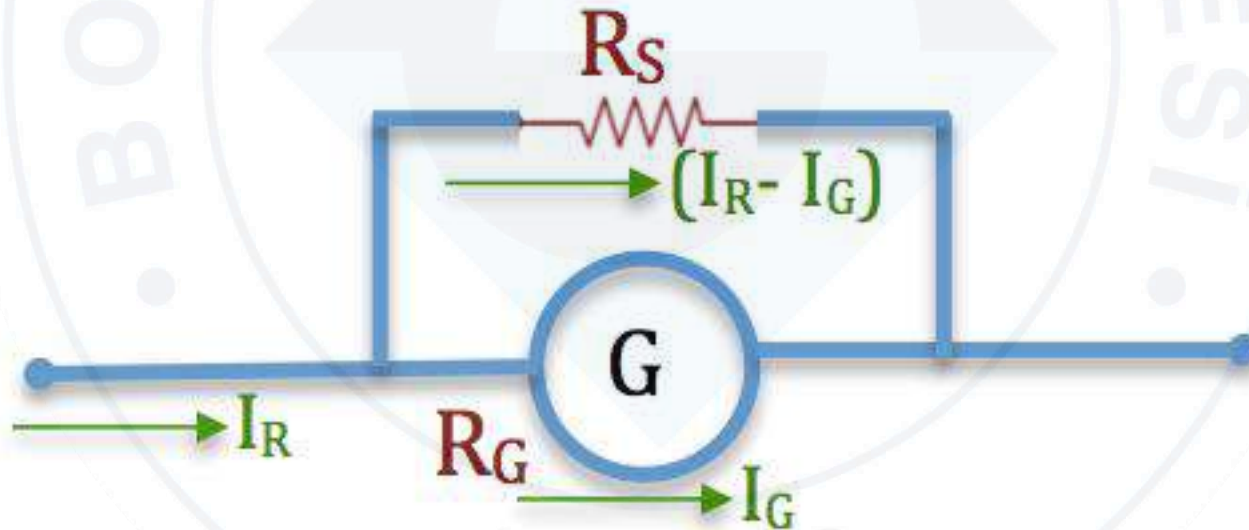Determine the value of  $R_S$ , the SHUNT RESISTANCE\*, that satisfies this condition.



\* Shunt means a component used to divert



## CONSTRUCTION OF AN AMMETER

Since  $R_S \ll 1\Omega$ , we will use as  $R_S$  a copper wire with resistance per unit length  $\rho_{CW} = 1.34 \times 10^{-3} \Omega/\text{cm}$ . Determine the length of the copper wire,  $L_{CW}$ , which will have a resistance  $R_S$ .

$$L_{CW} = ?$$



## CONSTRUCTION OF AN AMMETER

$$I_R = 1.0 \text{ A.}$$

$$\rho_{CW} = 1.34 \times 10^{-3} \text{ } \Omega/\text{cm}$$

*Please show your calculations in detail.*

Description / Symbol	Value & Unit
----------------------	--------------

Range for the Constructed Ammeter (*given*)  $I_R =$  .....

Resistance per unit length of the Copper Wire  $\rho_{CW} =$  .....

Description / Symbol	Calculation (show each step)
----------------------	------------------------------

Shunt Resistance  $R_S =$  .....

.....

Length of the Copper Wire  $L =$  .....

.....

## AMMETERS

### CONSTRUCTION OF AN AMMETER

A copper wire with the calculated length is connected in parallel to the galvanometer. This combination is our constructed ammeter, which measures a maximum of  $I_R$ .




CONSTRUCTED AMMETER


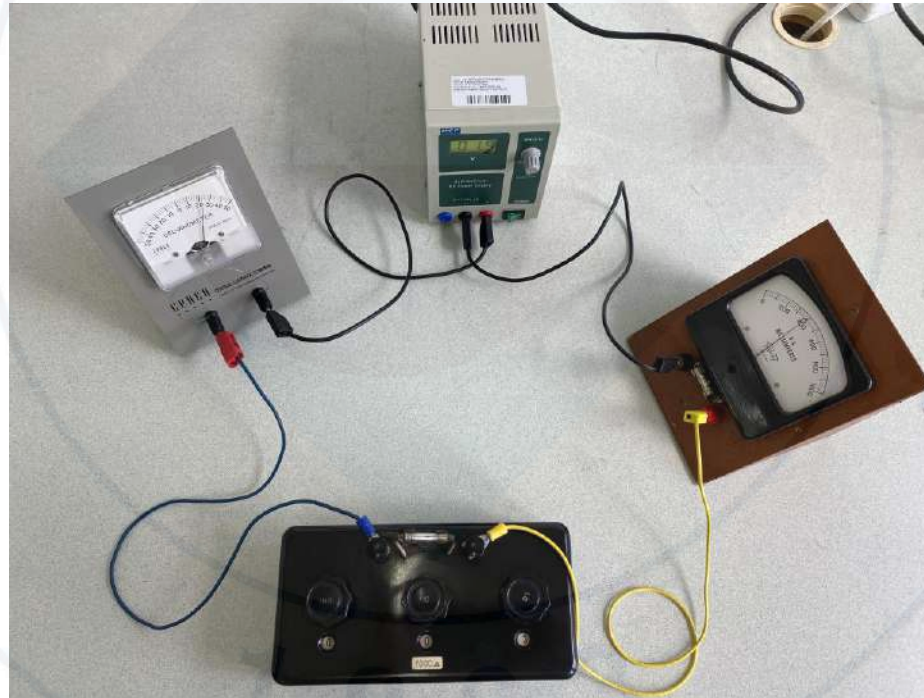
## CONSTRUCTION OF AN AMMETER

Now, we will test our constructed ammeter using a power supply and a  $2\Omega$  resistance.

Draw the circuit diagram to test the constructed ammeter in your work book.



TEST CIRCUIT FOR AMMETER

## CONSTRUCTION OF AN AMMETER

Use the photo given in the data video to read the current value on the real ammeter and read the scale on the constructed ammeter.

Then determine the ampere value of the constructed ammeter.





# AMMETERS

## CONSTRUCTION OF AN AMMETER

Calculate the ampere value of the constructed ammeter.

Calculate the percentage error.

Answer one of the questions 1 or 2 –of your choice– at the end of the experiment.

Description / Symbol	Value / Calculation	Result
Value read from the Galvanometer $I_x =$	.....	.....
Value read from the Constructed Ammeter $I_{EV} =$	.....	.....
	.....	.....
Value read from a Real Ammeter $I_{TV} =$	.....	.....
	.....	.....
<b>% Error for <math>I</math>:</b>		

# Part 3: Construction of a Voltmeter Procedure, Data, and Calculations

The following data are for demonstration purposes only.

In order to build a voltmeter, a sensitive galvanometer with an internal resistance of  $50\text{-}100\ \Omega$  is used.

Before we construct our measuring device, we need to know the exact internal resistance of the galvanometer, and what current causes Full Scale Deflection (FSD).



Full Scale Deflection occurs when the pointer shows the maximum value on the scale. Here, the maximum value is 50, and the galvanometer is Full Scale Deflected.

The current causing FSD is called the Galvanometer Current,  $I_G$ .

### CONSTRUCTION OF A VOLTMETER

We will construct a voltmeter that will measure a maximum of a given value  $V_R$ .

That means the galvanometer we use to build a voltmeter will Full Scale Deflect when we measure  $V_R$  volts.

We should remember that galvanometer current,  $I_G$ , causes Full Scale Deflection, and the voltmeter has a very high internal resistance.


## VOLTMETERS

### CONSTRUCTION OF A VOLTMETER

We will construct a voltmeter that will measure a maximum of  $V_R$ .

*$V_R$  will be given directly; you are not supposed to calculate it as shown in the book.*

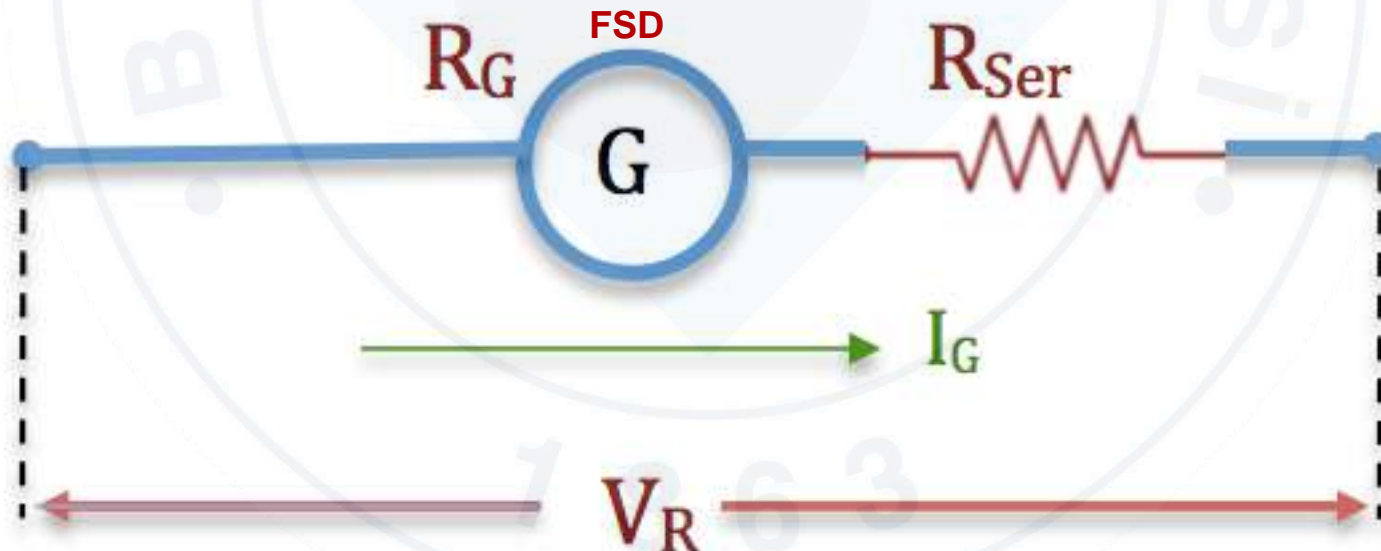What  $R_{Ser}$  value satisfies this condition? Determine  $R_{Ser}$ .





## CONSTRUCTION OF A VOLTMETER

We will construct a voltmeter that will measure a maximum of  $V_R$ .

What  $R_{Ser}$  value satisfies this condition? Determine  $R_{Ser}$ .

Description / Symbol	Calculation (show each step)	Result
Range for the Constructed Voltmeter $V_R$	$= 2.3 \text{ V} + \text{Table\#} / 10 =$	.....
Series Resistance	$R_{Ser} =$ .....	.....

# VOLTMETERS

## CONSTRUCTION OF A VOLTMETER

A resistance set to the calculated value  $R_{Ser}$  is connected in series to the galvanometer. This combination is our constructed voltmeter, which measures a maximum of  $V_R$  volts.




CONSTRUCTED VOLTMETER

# VOLTMETERS
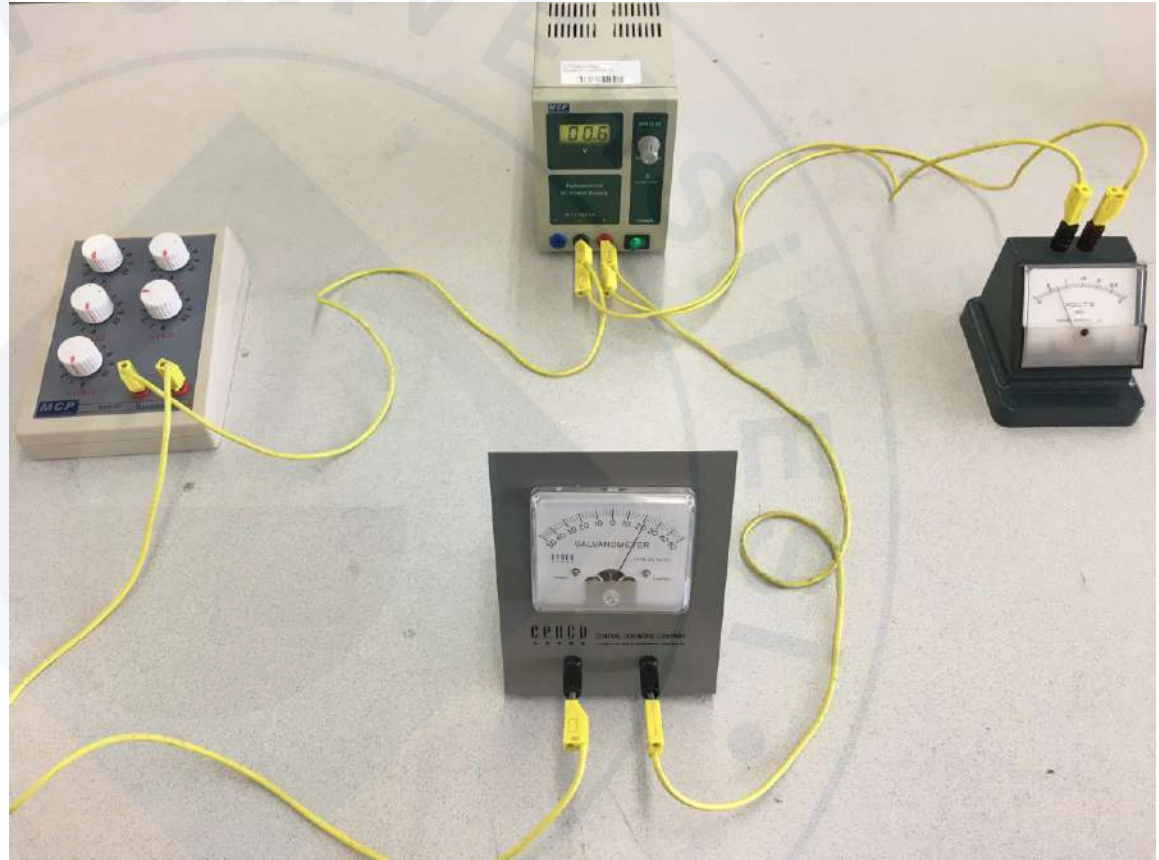
## CONSTRUCTION OF A VOLTMETER

Now, we will test our constructed voltmeter using a power supply.

Draw the circuit diagram to test the constructed voltmeter in your work book.



TEST CIRCUIT FOR VOLTMETER



## CONSTRUCTION OF A VOLTMETER

Use the photo given in the data video to read the voltage value on the real voltmeter and read the scale on the constructed voltmeter.

Then determine the voltage value of the constructed voltmeter.



## CONSTRUCTION OF A VOLTMETER

Calculate the voltage value given by the constructed voltmeter.

Calculate the percentage error.

Answer one of the questions 3 or 4 –*of your choice*– at the end of the experiment.

Description	Symbol	Value / Calculation	Result
Value read from the Galvanometer	$V_x =$	.....	.....
Value read from the Constructed Voltmeter	$V_{EV} =$	.....	.....
Value read from a Real Voltmeter	$V_{TV} =$	.....	.....

**% Error for  $V$ :**