



Boğaziçi University

**Introductory  
Phys Labs**

# **WHEATSTONE BRIDGE**

**PHYL 201**

1863

BOĞAZIÇI ÜNİVERSİTESİ


# THEORY

1863
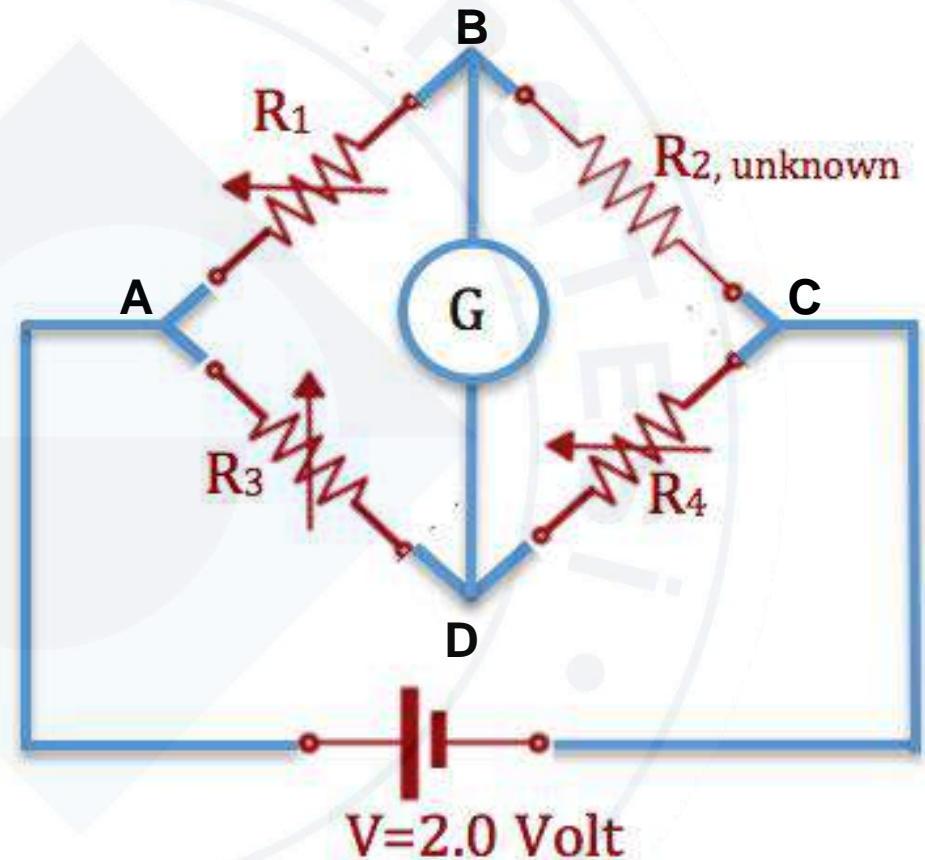
## WHEATSTONE BRIDGE

The Wheatstone Bridge is a combination of four resistances connected to give a null center value.

It was developed by Charles Wheatstone to measure unknown resistance values and as a means of calibrating measuring instruments, voltmeters, ammeters, etc., using a long resistive slide wire.




## WHEATSTONE BRIDGE

In Wheatstone bridge there are two pairs of resistors connected in parallel.



A galvanometer is connected between the points where individual resistors are connected together in each pair. To protect the galvanometer against excessive currents, a large resistance is connected in series with the galvanometer to short it out using a switch.

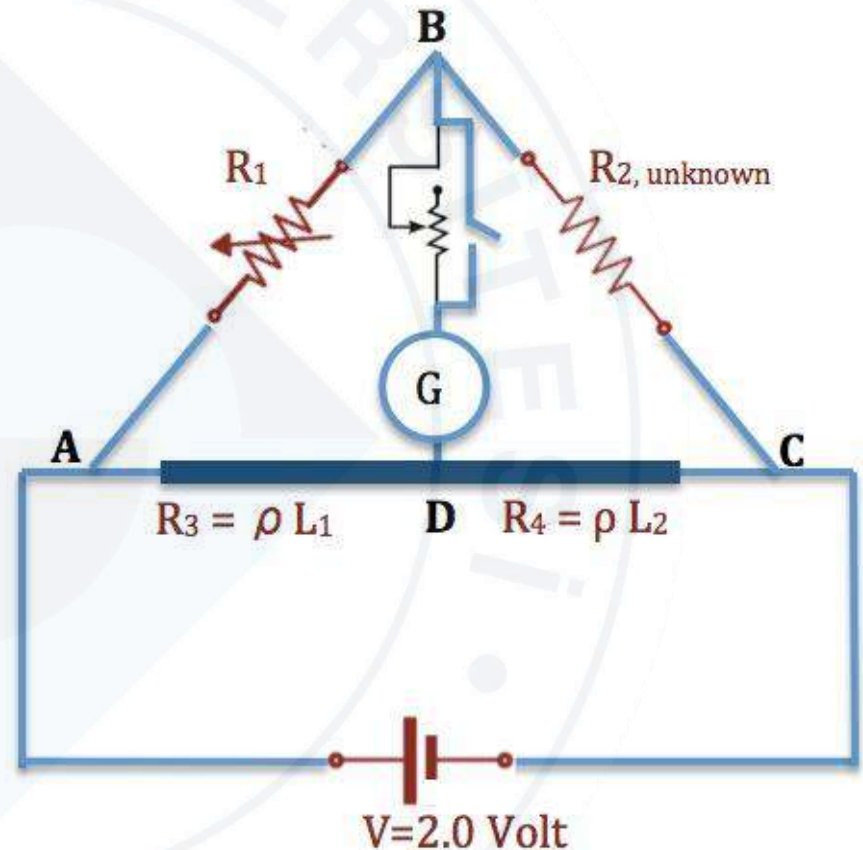In slide-wire Wheatstone Bridge case one pair of resistors is simply a wire and the galvanometer is connected to a point on the wire with the help of a sliding connection.



The Slide Wire Wheatstone Bridge

# WHEATSTONE BRIDGE

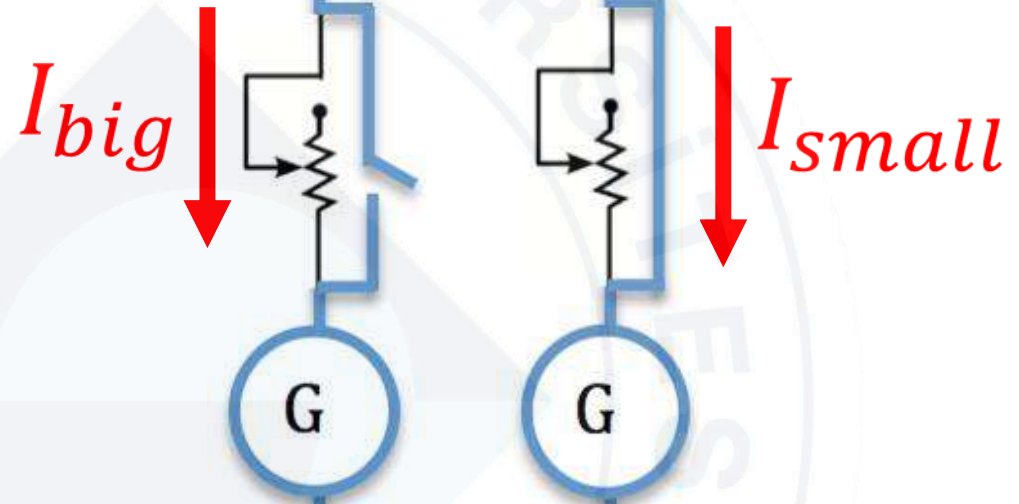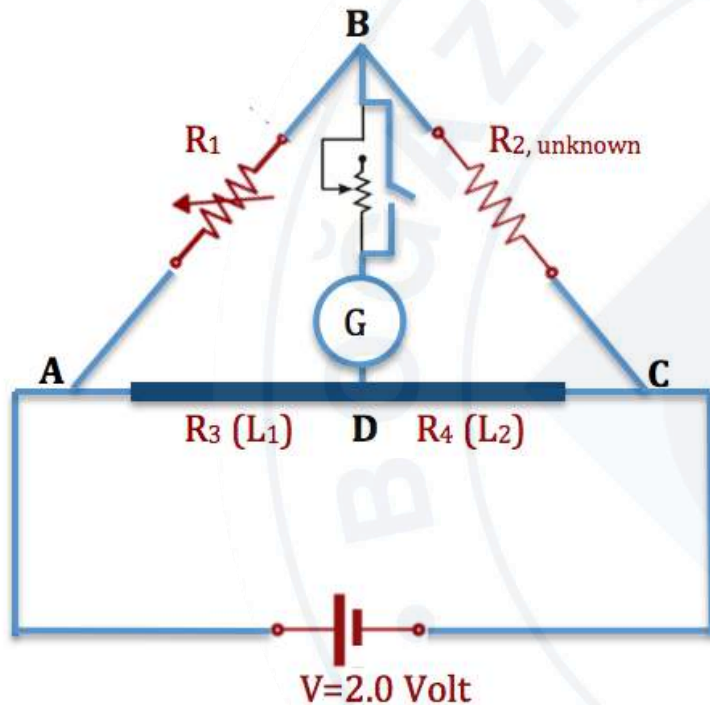

**Balance Condition:**

$$I = 0$$
$$V_B = V_D$$

The Slide Wire Wheatstone Bridge



## WHEATSTONE BRIDGE

The galvanometer is the device used for detecting the presence of a small current or a small voltage.

The galvanometer has following applications:

- It is used for detecting the direction of current flows in the circuit. It also determines the null point of the circuit. The null (zero) point means the situation in which no current flows through the circuit.
- It maybe used for measuring a very small current.
- The voltage between any two points of the circuit may also be determined by using a galvanometer.




# WHEATSTONE BRIDGE

Assuming that the resistances in the wire part of the circuit are  $R_3$  and  $R_4$  and the other part are  $R_1$  and  $R_2$ .

Then, adjusting the position of the sliding contact on the wire, the current through the galvanometer is brought to zero, namely

$$V_B = V_D$$

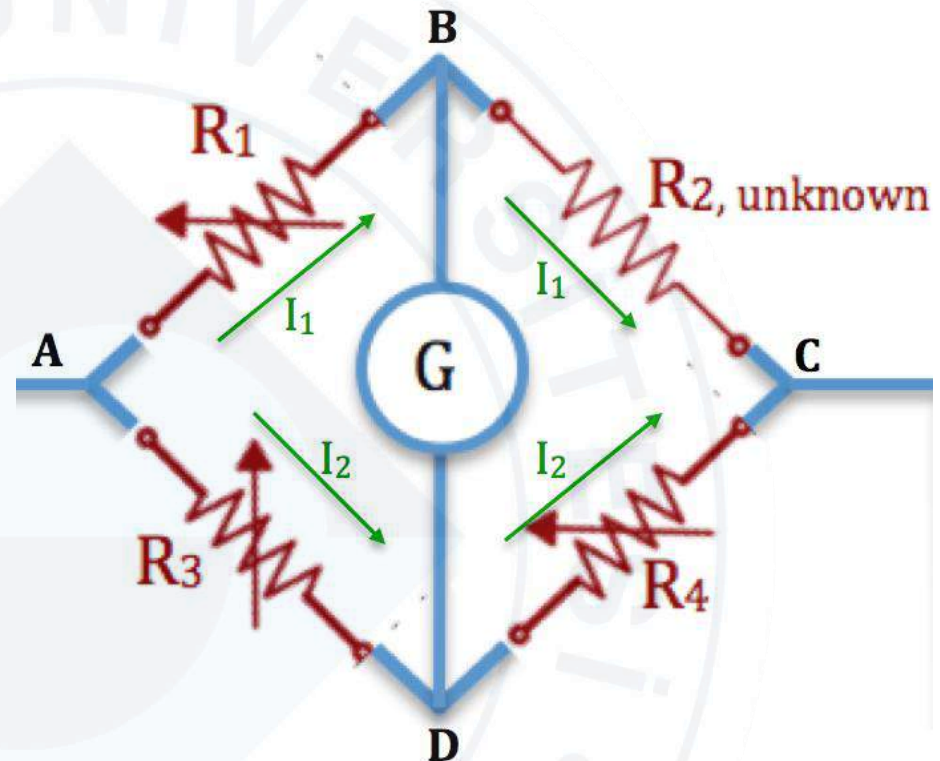The current passing through the wire part is  $I_2$  and the other part is  $I_1$ .



$$V_{AB} = V_{AD}$$

$$V_{BC} = V_{DC}$$



## WHEATSTONE BRIDGE

This means that the potential differences across the resistances opposing each other in each pair will be equal:

$$V_{AB} = V_{AD} \quad \longrightarrow \quad I_1 R_1 = I_2 R_3$$


$$V_{BC} = V_{DC} \quad \longrightarrow \quad I_1 R_2 = I_2 R_4$$

Dividing the first expression by the second one, we get

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} = \frac{L_1}{L_2}$$

$$L_2 = 100 - L_1 \quad (\text{we measure } L_1)$$
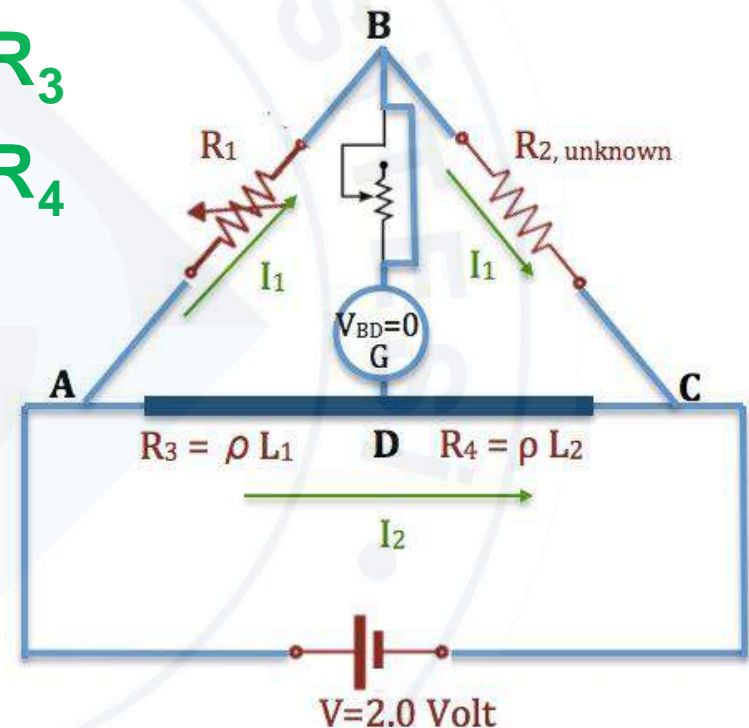
$$R_2 = R_{\text{unknown}} = (L_2/L_1) R_1 = [(100-L_1)/L_1] R_1$$



The background features a large, faint watermark of the Boğaziçi University logo. It consists of a circular emblem with the text "BOĞAZIÇI ÜNİVERSİTESİ" around the top and "1863" at the bottom. In the center of the emblem is a stylized geometric design, possibly representing a building or a symbol.

# **EXPERIMENT SETUP AND METHOD**


## WHEATSTONE BRIDGE

There are 5 different unknown resistors. We will connect those in place of  $R_2$  in the Wheatstone Bridge circuit.


All 5 resistors are connected in series on the board.



# WHEATSTONE BRIDGE

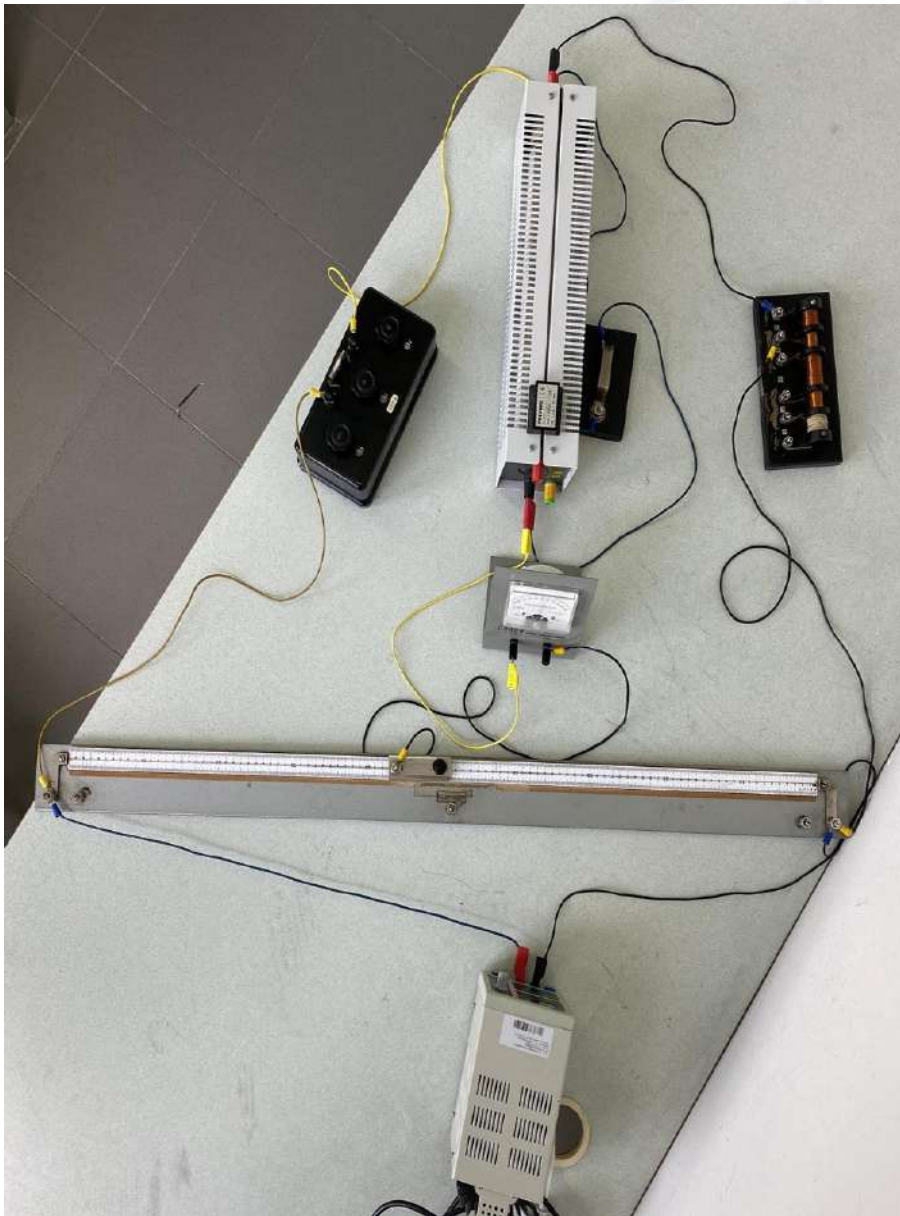


Here is the circuit in detail:

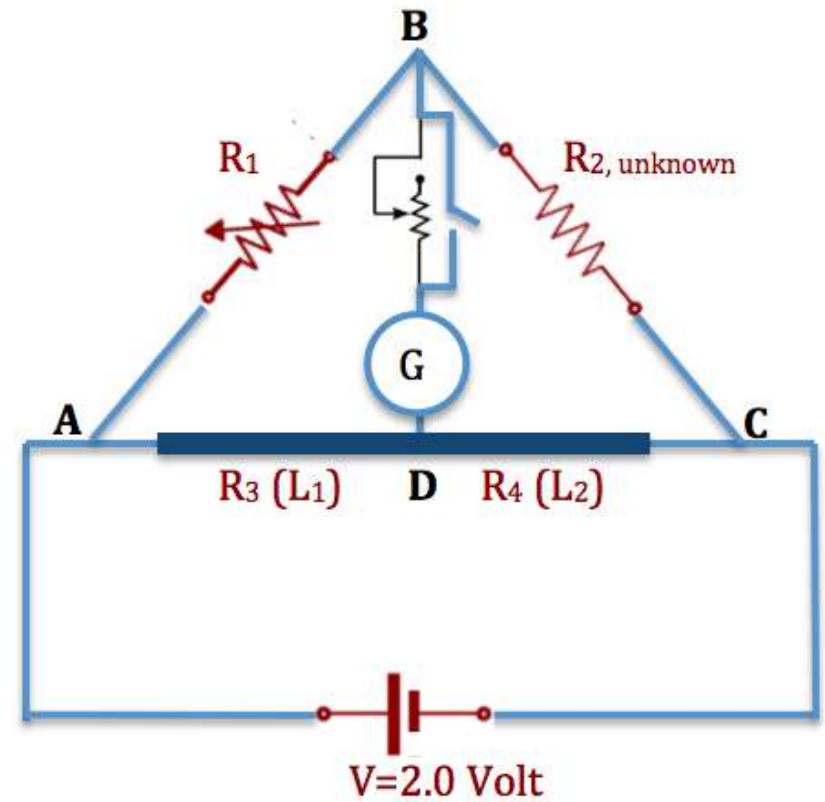


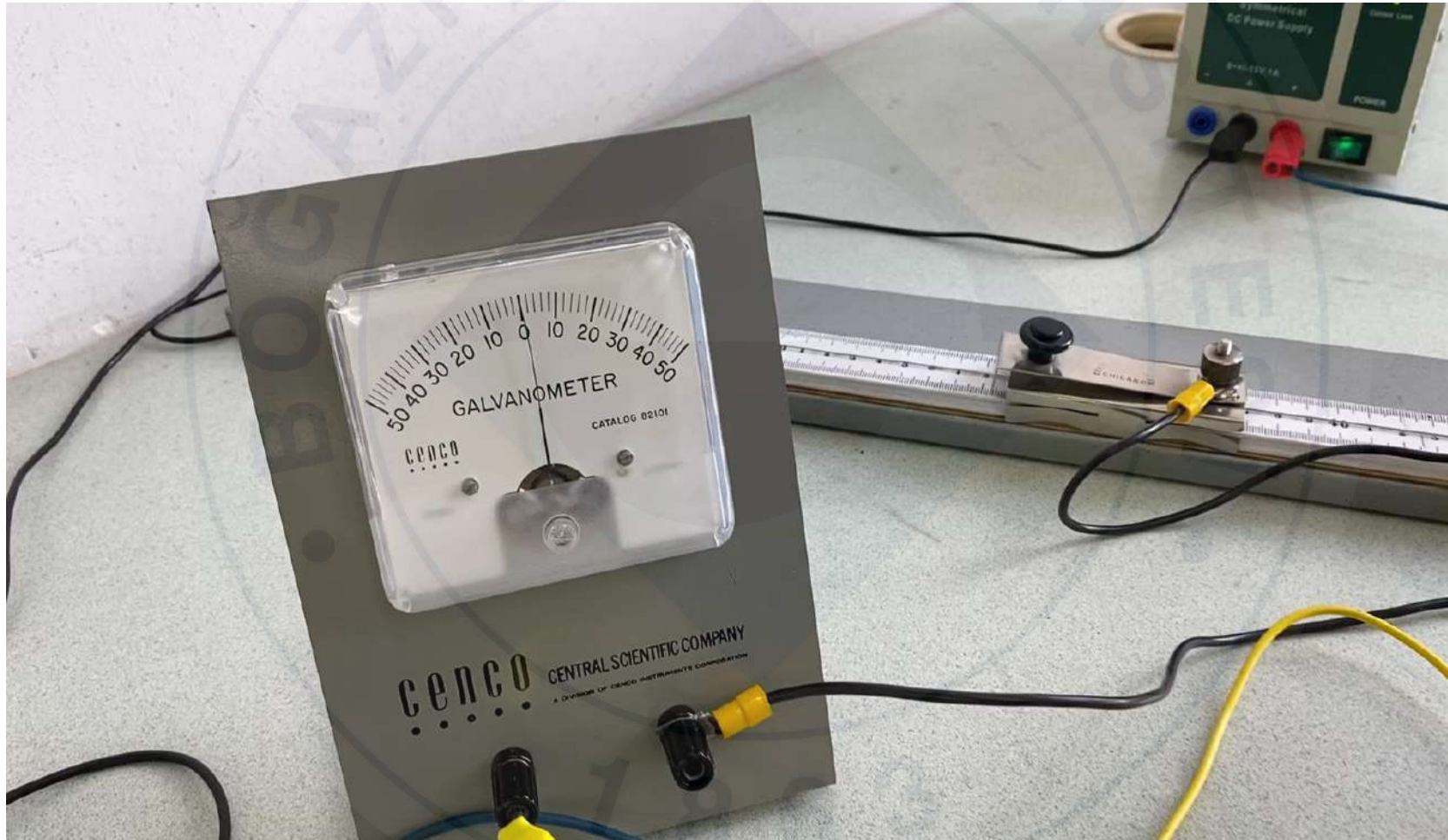
## WHEATSTONE BRIDGE

Adjusting the position of the sliding contact on the wire, the current through the galvanometer is brought to zero.





A large, faint, light blue watermark of the Boğaziçi University seal is centered in the background. The seal is circular and contains the text "BOĞAZIÇI ÜNİVERSİTESİ" around the top and "1863" at the bottom. In the center of the seal is a diamond shape with a smaller diamond inside it, and a circle in the middle of the inner diamond.

# DATA-TAKING

# WHEATSTONE BRIDGE

Record your readings into table.

## DATA-TAKING


Name of the Resistance*	$R_1$ ( )	$L_1^{**}$ ( )	$L_2$ ( )
	(Resistance Box)	# of Significant Figures =	# of Significant Figures =
$R_A$			
$R_B$			
$R_C$			
$R_{\text{Series}}$ (A and C)			
$R_{\text{Parallel}}$ (A and C)			

\* Ignore unknown resistances D and E!  $R_1$  can be different for different unknown resistances.

\*\*  $L_1$  should be in the interval  $10.0 \text{ cm} < L_1 < 90.0 \text{ cm}$ . Otherwise, change  $R_1$  and retry!

# WHEATSTONE BRIDGE

**SAMPLE**

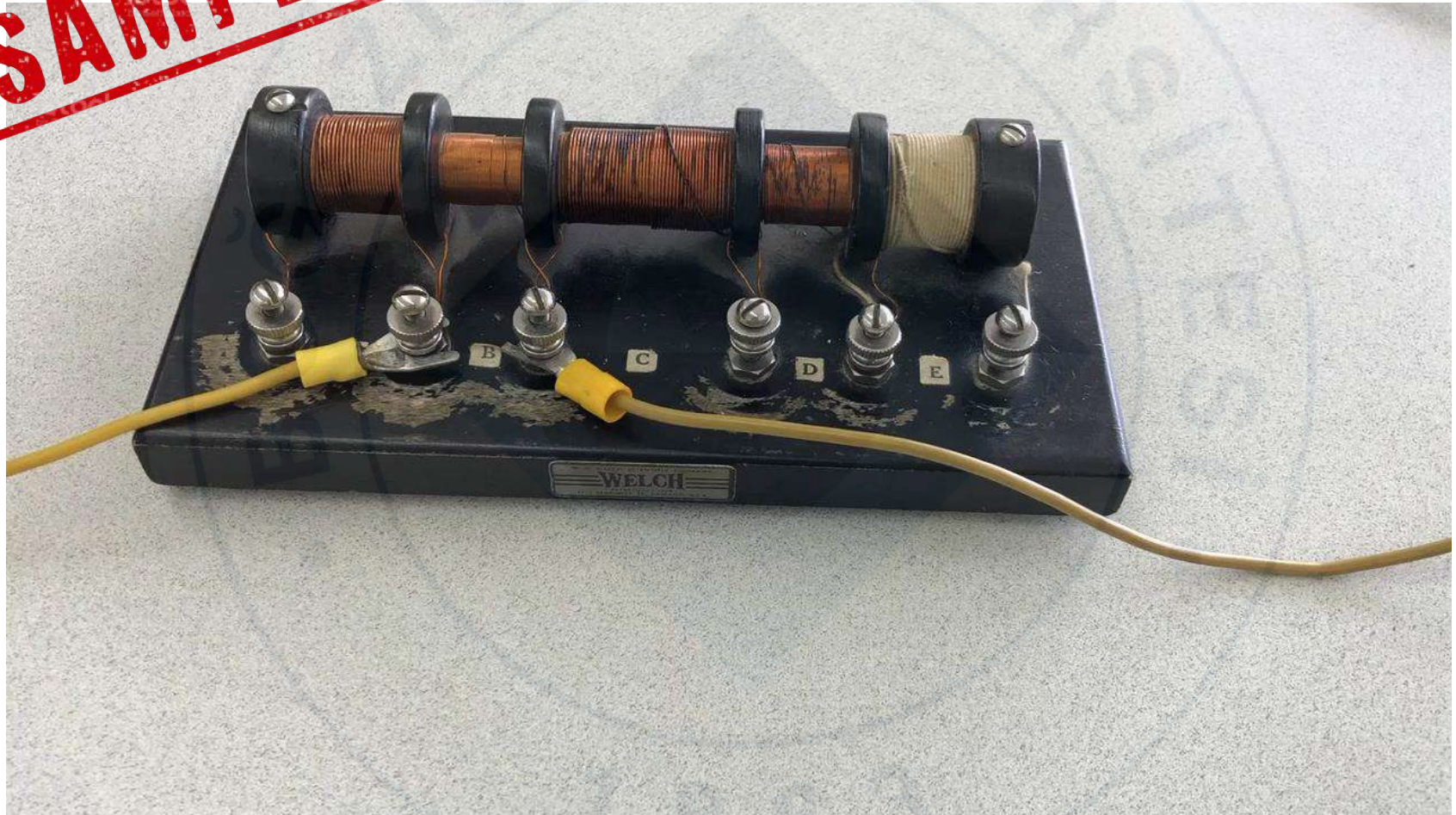

# **SERIES CONNECTION OF 2 RESISTORS**



## WHEATSTONE BRIDGE

Series connection:  $R_{\text{ser}} = R_A + R_C$






# PARALLEL CONNECTION OF 2 RESISTORS
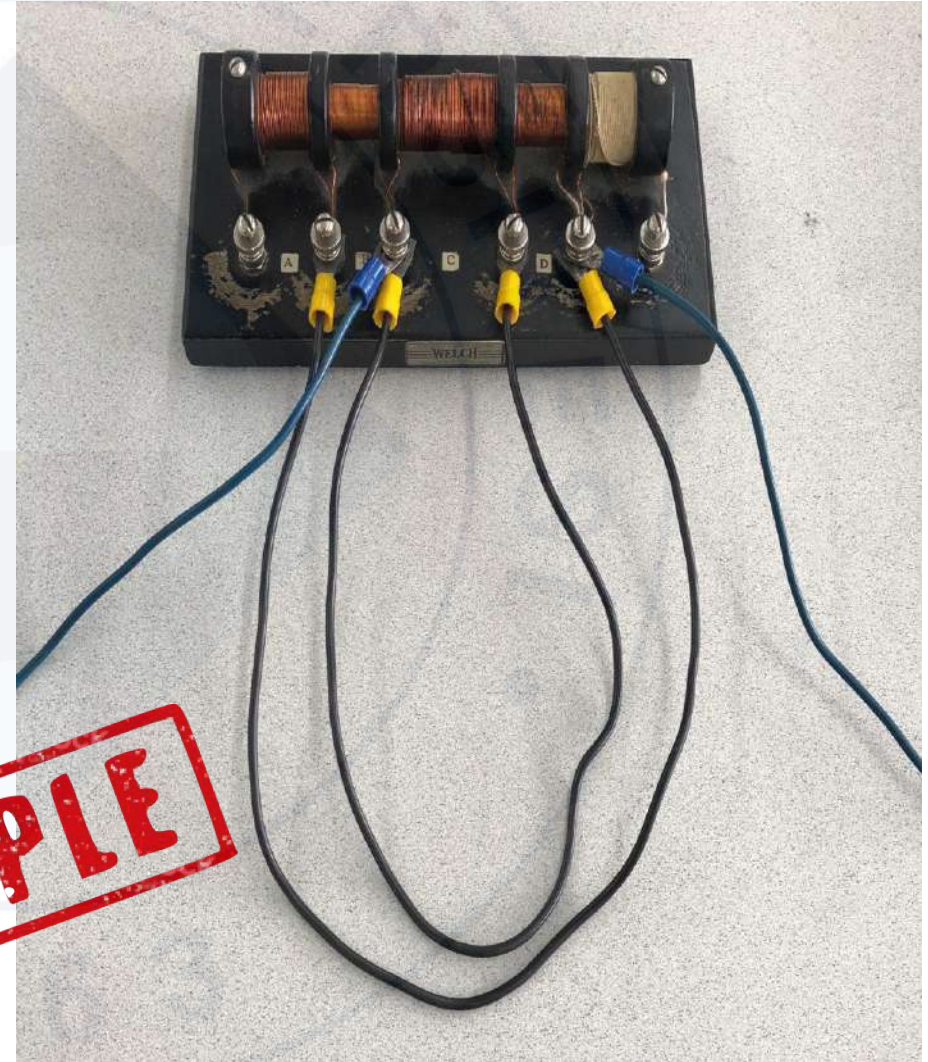
# WHEATSTONE BRIDGE

Parallel connection:  $1/R_{\text{parallel}} = 1/R_B + 1/R_D$



The background features a large, light blue watermark of the Boğaziçi University logo. The logo is circular and contains the text "BOĞAZIÇI ÜNİVERSİTESİ" around the top edge and "1863" at the bottom. In the center of the logo is a diamond shape with a circle inside it.

# **CALCULATIONS**

## CALCULATIONS

<u>Symbol</u>	<u>Calculations (show each step)</u>	<u>Result</u>
$R_A =$	.....	.....
$R_B =$	.....	.....
$R_C =$	.....	.....
$R_{\text{Series}} =$	.....	.....
$R_{\text{Parallel}} =$	.....	.....

$$R_x = \frac{(100.0 - L_1)}{L_1} R_1$$

Use this formula to calculate each of the unknown resistances.



# WHEATSTONE BRIDGE

## CALCULATIONS

<u>Symbol</u>	<u>Calculations (show each step)</u>	<u>Result</u>
---------------	--------------------------------------	---------------

$R_{\text{series}} =$ (expected)	.....	.....
-------------------------------------	-------	-------

$R_{\text{parallel}} =$ (expected)	.....	.....
---------------------------------------	-------	-------

Use the theoretical formulae for equivalent resistance to calculate

## RESULTS

% Error for $R_s$ :	.....	.....
---------------------	-------	-------

% Error for $R_{//}$ :	.....	.....
------------------------	-------	-------

Accept the expected values as the true values